

www.ankurgupta.net

## Digital Logic

(1) Range of  $n$  bit 2's complement number:-

$$\dots -2^{(n-1)} \text{ to } (2^{(n-1)} - 1)$$

(2) Range of  $n$  bit 1's complement number:-

$$-(2^{(n-1)} - 1) \text{ to } (2^{(n-1)} - 1)$$

(3) Implicant:-

A normal product term that implies  $Y$ .

$$Y = \underbrace{AB + ABC + BC}_{\text{Implicants}}$$

(4) Prime Implicants:-


An implicant of  $Y$  such that if any variable is removed from the implicant, the resulting term does not imply  $Y$ .

$$Y = \underbrace{AB + BC}_{\text{Prime Implicant}} + ABC \rightarrow \text{Not a prime implicant.}$$

(5) Essential Prime Implicant:-


If a minterm is covered only by a prime implicant, then this prime implicant is called an essential prime implicant.

 (6) Finite State Machine to calculate 2's complement:-



### S-R (Set-Reset) Flip-Flop

S(1)	R(1)	Q(1)	Q(1+E)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

 

- } inputs not allowed  
- }


Characteristic Equation:-

$$Q^+ = S + R'Q$$

(SR=0)  
↳ Condition for both of the inputs to be complied

### D (delay) Flip-Flop:-

D	Q	Q <sup>+</sup>
0	0	0
0	1	0
1	0	1
1	1	1

 


Characteristic Equation:-

$$Q^+ = D$$

### T (Trigger) Flip-Flop:-

T	Q	Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0

 


Characteristic Equation:-

$$Q^+ = T'Q + TQ' = T \oplus Q$$

### JK Flip-Flop:-

J	K	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 

Characteristic Equation:-

$$Q^+ = QK' + Q'J$$


Characteristic Equation:-

An equation which expresses the next state of a flip-flop in terms of its present state and inputs.


 
## Clocked Flip-Flops with Clear and Preset Inputs:-

- # A 0 applied to the clear input will reset the flip-flop to  $Q=0$



- # A 0 applied to the preset input will set the flip-flop to  $Q=1$


- # These inputs override the clock and J-K inputs

## Moore Machine:-


If the output of a sequential network is a function of the present state only, the network is often referred to as a Moore Machine.
 
## Mealy Machine:-

If the output is a function of both the present state and the input, the network is referred to as a Mealy Machine.



Moore Machine

 

Mealy Machine

## Positive Logic:-

+V represent a logic 1 and 0 volts represent a logic 0.

## Negative Logic:-

+V represent a logic 0 and 0 volts represent a logic 1.

## Finding the minimum number of Gates, required to solve an expression:-


To find a minimum solution, one must find both the network with the AND-gate output and the one with the OR-gate output.

## Multiplexers:-

A multiplexer has a group of data inputs and a group of control inputs.

The control inputs are used to select one of the data inputs and connect it to the output terminal.
 
$$Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$




# A  $2^n$  to 1 multiplexer can be used to realize any  $(n+1)$  variable function with no-added gates.  $n$  of the variables are used as control inputs and the remaining variable is used as required on the data inputs.


 
### Decoders:-

A decoder is a combinational logic circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.



### Encoders:-

An encoder is a combinational logic circuit. It is reverse of decoder function. It has  $2^n$  (or fewer) input lines and  $n$  output lines.

### Multiplexer Applications:-

- (1) Data Routing
- (2) Function Generator
- (3) Parallel to Serial Conversion

### Demultiplexer Applications:-

- (1) Serial to Parallel Conversion.

### Shift Register Applications:-

- (1) Time delay
- (2) Serial to parallel data converter
- (3) Parallel to serial data converter

### Canonical Logic Forms:-

If each term in SOP and POS forms contain all the literals then these are known as Canonical (Standard) SOP and POS expression.


### Half Adder:-

$$\begin{aligned} S &= A \oplus B \\ C &= AB \end{aligned}$$


 
### Full Adder:-

$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ C_{out} &= (A \oplus B)C_{in} + AB \end{aligned}$$



### Look Ahead Carry Adder:-

$$\begin{aligned} S_i &= P_i \oplus C_i \\ C_{i+1} &= G_i + P_i C_i \end{aligned} \quad \begin{cases} P_i = A_i \oplus B_i \\ G_i = A_i \cdot B_i \end{cases}$$

$$i=0$$

$$C_1 = G_0 + P_0 C_0$$

$$i=1$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \end{aligned}$$

$$i=2$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 (G_0 + P_0 C_0)) \end{aligned}$$

$$i=3$$


$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 (G_1 + P_1 (G_0 + P_0 C_0))) \end{aligned}$$



### Half Subtractor :-

$$D = A \oplus B$$


$$B_{out} = \bar{A}B$$

 
 
### Full Subtractor :-

$$D = A \oplus B \oplus B_{in}$$


$$B_{out} = (A \oplus B)B_{in} + \bar{A}B$$



### Binary Code to Gray Code Conversion :-

Binary Code -


Gray Code -

 

### Gray Code to Binary Code Conversion :-

Gray Code -

Binary Code -

 

### Reduction of State Tables :-

- (1) Elimination of Redundant States
- (2) Determination of State Equivalence using an Implication Table.

Implication Table

	A	B	C
A	<del>A-A</del>	<del>A-B</del>	<del>A-C</del>
B	<del>B-A</del>	<del>B-B</del>	<del>B-C</del>
C	<del>C-A</del>	<del>C-B</del>	<del>C-C</del>
D	X	X	X

Annotations:   
 - A=B, if A=D & B=C   
 - C ≠ D since output differ   
 - Next State q/p

$$B \equiv C$$

### New State Table :-

	0	1
A	D, 0	B, 1
B	A, 0	B, 1
D	A, 1	B, 1